



LAPP - Annecy - October 2000

The Front-End electronics for LHCb calorimeters

Christophe Beigbeder - LAL Orsay

On behalf of the LHCb calorimeter team







LHCb calorimeter main features

- The calorimeter system is used in several stages for Level 0 and Level 1 triggers and off-line analysis
 - Provide hadrons, photons and electrons candidates
 - Measurement of their energy and position .
 - Selectivity and fast response
 - Provide identification of photons
 - Good background rejection
 - Preshower detector
- □ High level0 rate , high occupancy
 - ▶ Full information every 25 ns
 - ▶ Level0 yes possible every 25 ns
- \square Cost/performance compromise.
 - Ecal based on Shashlik technology.
 - Scintillating tile geometry for the Hcal. ٠
 - Common front-end electronics for Ecal and Hcal

LHCD ГНСР







The LHCb calorimeters and muon chambers

Requirements for the calorimeter front-end electronics

- □ Provide a fast signal :
 - ↓ Fast Pms covering the whole dynamic range of the 2 calorimeters
 - ↓ WLS Fibers with fast decay time
- □ Shape the input signals from PMs with total pile-up independence
- □ Perform analog to digital conversion on 12 bits at 40 MHz
- □ Perform a LF noise rejection
- □ Convert data into energy thanks to LUTs for trigger and readout
- □ Buffer data during the Level0 trigger latency
- □ Derandomize and buffer data during the Level1 trigger latency
- □ Perform a event formatting
- □ Look for local energy maxima over the channels
- □ Send the trigger information to the Trigger Validation Boards







Measurement of the pulse shape properties using both X7 test beam and ultra violet N2 laser





Results of fiber study









Hcal prototype overview









Front_End elements



- □ Purpose :
 - ∠ To shape PM pulses in less than 25ns to avoid electronics pile-up.
- □ Specifications :
 - ✓ Input Signal 20mA over 25₩
 - ∠ Dynamic Range : 1V at the input of the ADC (250 W)
 - ∠ Residue < 2% after 25ns.
 - ∠ Sampling with 1% precision over +/- 3ns after shaping.
 - \checkmark RMS Noise < 1 ADC Count (i.e. 250 .v)

гнср



Simulated Input Signal



Principle of the Integrator Filter



BiCMOS 0.8um ASIC 4 Channels per chip







▶ Strobe on the flat top (» 10ns).

▷ Shaping : h(t) = [i(t) - i(t+25ns)] dt



Lнср гнср





Both signals have been sampled by digital oscilloscope

Integrator Filter performances on test bench

Simulation Resu	ults : Current	Test Bench Results :
Dynamic Range : 1.4V	<=>	1.4V
Non Linearity : 0.5%	<=>	$<\!1\%$
Residue after 25 ns : <0.5%	<=>	<1%
RMS Noise after subtraction		
1 Adc count	<=>	1.1 Adc count
Power Consumption : 40mW /	/ Channel <=>	38mW / Channe
Open-Loop Gain : ~60dB	<=>	~6 0dB
gm (Input PMOS) = 34mA / V	/ <=>	18mA / V
Fall Time : 3us	<=>	2us
Rise Time (?) : 2.5ns	<=>	<u> 5</u> ns
Input Impedance : 190W	<=>	270 W







Block diagram of the baseline subtractor





Top view of the 16 channel prototype front-end board









Bottom view of the 16 channel prototype front-end board









Front-end Board versus LeCroy ADCs



Test beam results



Trigger related operations on Front-End Board

- □ Operations on Front-End board
 - ▷ ADC data converted to 8 bits in a Look-Up Table (LUT)
 - Allows any coding. But should be additive
 - We foresee to use E_T coded on 8 bits, up to 5.12 GeV by .02 GeV steps
 - ▷ Data is sent to neighbors
 - on the card
 - via the backplane
 - => takes only one clock cycle.
 - or via short, serially multiplexed
 - LVDS intercrate lines
 - => could take more than one clock cycle.
 - ▷ Data is summed 2 by 2 in vertical lines
 - ▷ These sums are summed 2 by 2 in horizontal lines
 - ▷ The 32 sums (clusters) are compared and the highest one selected
 - Performed by a pyramid of "compare and select"
 - Should fit in 6 steps if the 45 energies enter the same big FPGA (~400I/O)
 - Currently fits in 10 steps within 4 "smaller" FPGAs
 - Confirmed by Verilog simulations
 - Could probably fit in 8 steps (under study)









Next steps of the developments

- Board design : Validation board (trigger concentrator), CROC (Crate and Readout Controller) and Backplane.
- □ Technical points :
 - ▶ Study on LVDS signals from 10MHz@100m to 280MHz@10m.
 - ▷ SEU problems :
 - More precise knowledge of the radiation environment required.
 - Board test setup for proton/neutron irradiation.



